

ECSE 543 Assignment 1

Garrett Kinman – 260763260

Question 1

- a) Write a program to solve the matrix equation $Ax=b$ by Choleski decomposition. A is a real, symmetric, positive-definite matrix of order n .

One function was created to solve $Ax=b$ with Choleski decomposition with function signature shown below. The rest of the function body can be found in the appendix.

```
"""
Uses Choleski decomposition to solve `Ax = b`, where A is real, symmetric,
and positive-definite. Returns the vector x.
"""
function choleski(A::AbstractMatrix{<:Real}, b::AbstractVector{<:Real})
```

- b) Construct some small matrices ($n = 2, 3, 4$, or 5) to test the program. Remember that the matrices must be real, symmetric, and positive-definite. Explain how you chose the matrices.

Two example positive-definite matrices were chosen, one 2×2 and one 3×3 . These were provided in the Wikipedia page on positive-definite matrices as examples. Because, as mentioned in lectures, successful Choleski decomposition of a matrix is the best proof of its positive-definiteness, only checks for squareness and real-ness were added in the function itself. The two matrices chosen are shown below. Of note is that the first one is simply a 2×2 identity matrix.

```
[1 0
 0 1]
```

```
[2 -1 0
 -1 2 -1
 0 -1 2]
```

- c) Test the program you wrote in (a) with each small matrix you built in (b) in the following way: invent an x , multiply it by A to get b , then give A and b to your program and check that it returns x correctly.

The Choleski decomposition function was tested with a set of unit tests. For each test A matrix, a simple test case was performed, then a series of 10 randomized x vectors were used. The results and the code are shown below. One thing to note is that using simple equality returned an error whenever the result was floating point, because of floating-point errors in the calculations. Because of this, a built-in Julia operator for approximate equals (an operator built with the express purpose of accounting for floating-point errors) was used.

Test Summary:		Pass	Total
real, symmetric, and positive-definite		22	22

```
@testset "real, symmetric, and positive-definite" begin
    # test a simple 2x2 case
    test_A = [1 0; 0 1]
    test_x = [1; 1]
    test_b = test_A * test_x
    @test choleski(test_A, test_b) ≈ test_x # approx is to account for
    floating point errors

    # test 10 random 2x2 cases
    for i ∈ 1:10
        test_x = rand(2)
        test_b = test_A * test_x
        @test choleski(test_A, test_b) ≈ test_x
    end

    # test a simple 3x3 case
    test_A = [2 -1 0; -1 2 -1; 0 -1 2]
    test_x = [1; 1; 1]
    test_b = [1; 0; 1]
    @test choleski(test_A, test_b) ≈ test_x

    # test 10 random 3x3 cases
    for i ∈ 1:10
        test_x = rand(3)
        test_b = test_A * test_x
        @test choleski(test_A, test_b) ≈ test_x
    end
end
```

- d) Write a program that reads from a file a list of network branches (Jk, Rk, Ek) and a reduced incidence matrix, and finds the voltages at the nodes of the network. Use the code from part (a) to solve the matrix problem. Explain how the data is organized and read from the file. Test the program with a few small networks that you can check by hand. Compare the results for your test circuits with the analytical results you obtained by hand. Clearly specify each of the test circuits used with a labeled schematic diagram.

Circuit configurations were stored as standard *.toml* files, which indicates them as using *Tom's Obvious, Minimal Language*, a simple markup language. An example of the structure of the files is shown below.

```
num_nodes = 1
num_branches = 2
A = [ [ -1, 1 ] ]
J = [ 0, 0 ]
R = [ 10, 10 ]
E = [ 10, 0 ]
```


To parse the files, a Julia package for parsing TOMLs, *TOML.jl*, was used. The arrays as parsed by the *TOML.jl* packages were interpreted into vector or matrix datatypes as appropriate, in order to perform the necessary calculations. A function was then written for solving a given circuit, which calls the above function for Choleski decomposition. The function signature is given below, and the full function body is in the appendix.

```
"""
Solves a circuit given the reduced incidence matrix, A; current source
matrix, J;
resistance matrix, R; and voltage source matrix, E. Solves using Choleski
decomposition.

Tip: use the spread operator, `...`, to use the returned output of
`get_circuit(id)`
without having to access the members of the named tuple.
"""
function solve_circuit(A, J, R, E)
```

Following are the circuits it was tested on, as well as the results.


Circuit 1:

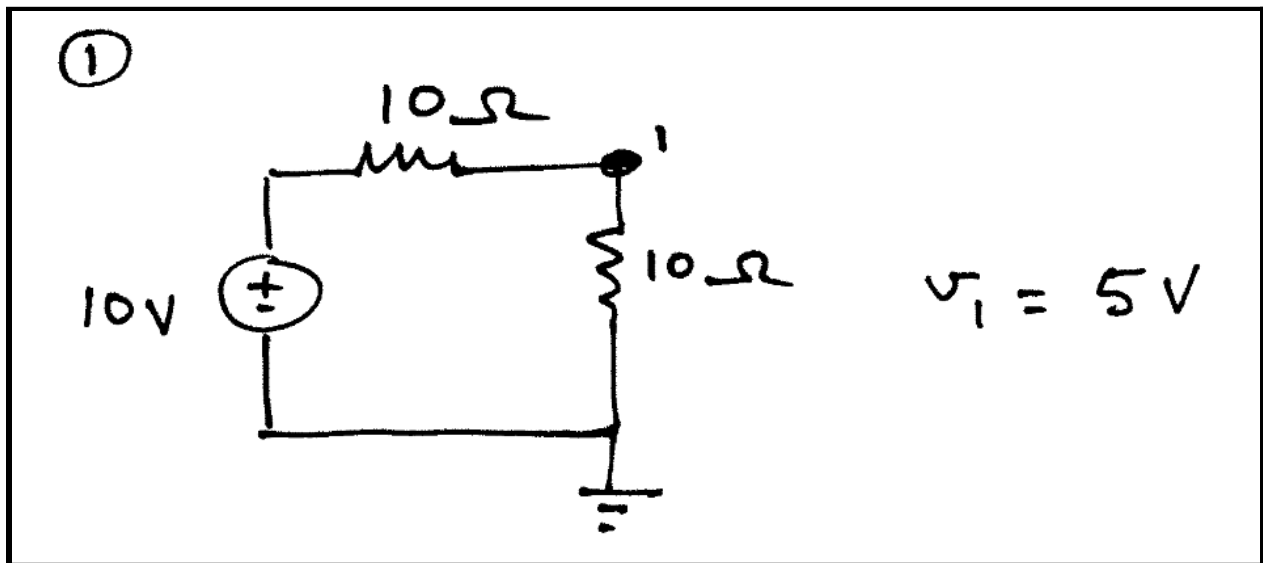

Result:

```
julia> solve_circuit(circuit1...)
1×1 Matrix{Float64}:
 5.0
```

Circuit 2:

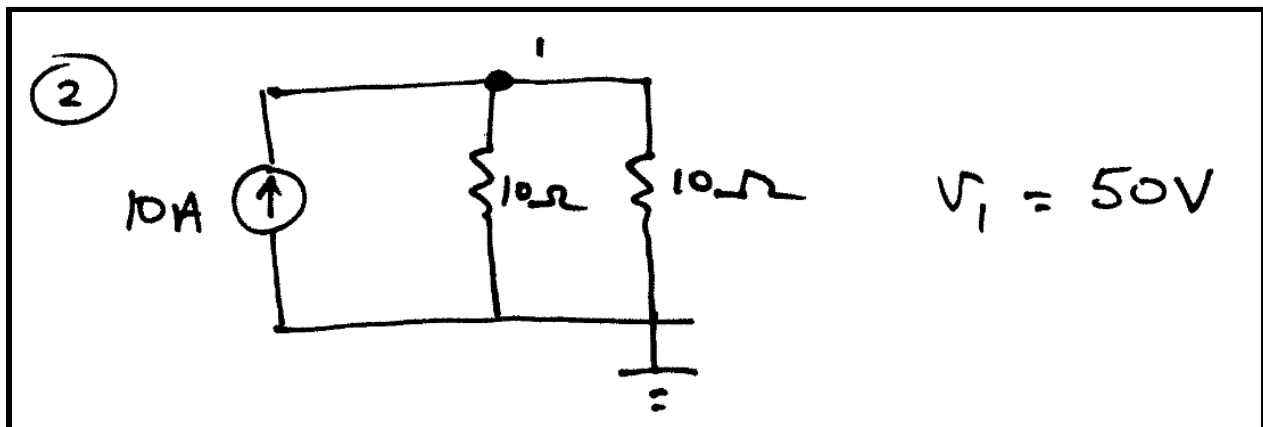


Result:

```
julia> solve_circuit(circuit2...)
1×1 Matrix{Float64}:
 50.00000000000001
```

Note the floating-point error here; this is what the approximate equals operator was used for in the unit tests.


Circuit 3:

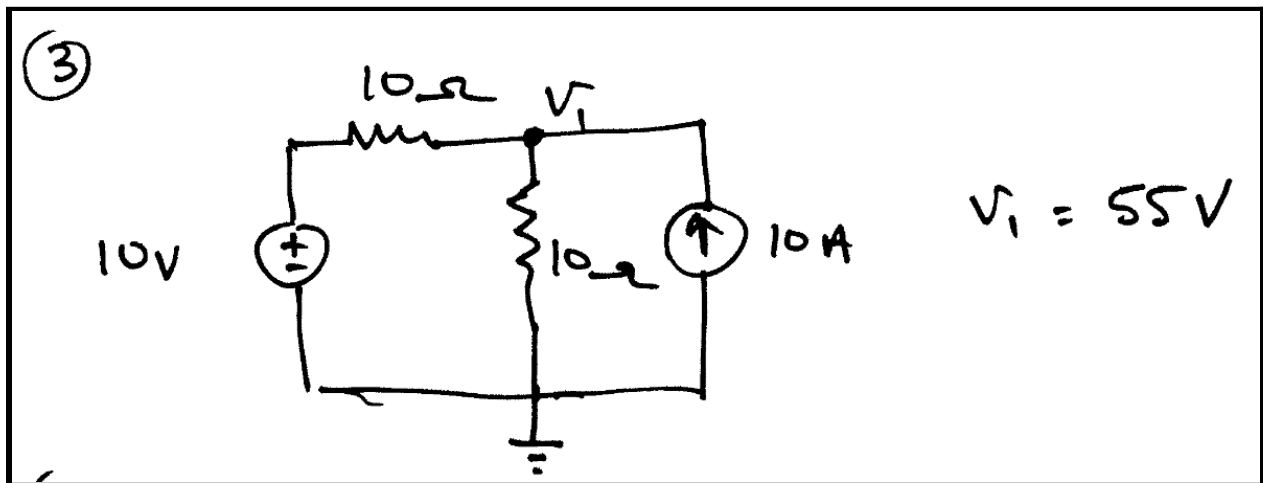

Result:

```
julia> solve_circuit(circuit3...)
1×1 Matrix{Float64}:
55.00000000000001
```


Circuit 4:

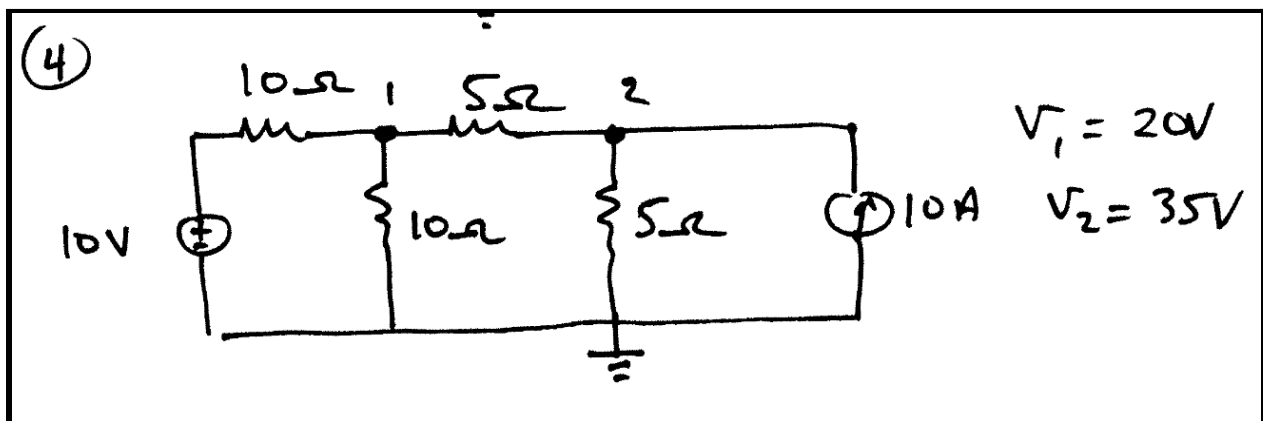

Result:

```
julia> solve_circuit(circuit4...)
2×1 Matrix{Float64}:
19.999999999999993
34.999999999999986
```

Circuit 5:

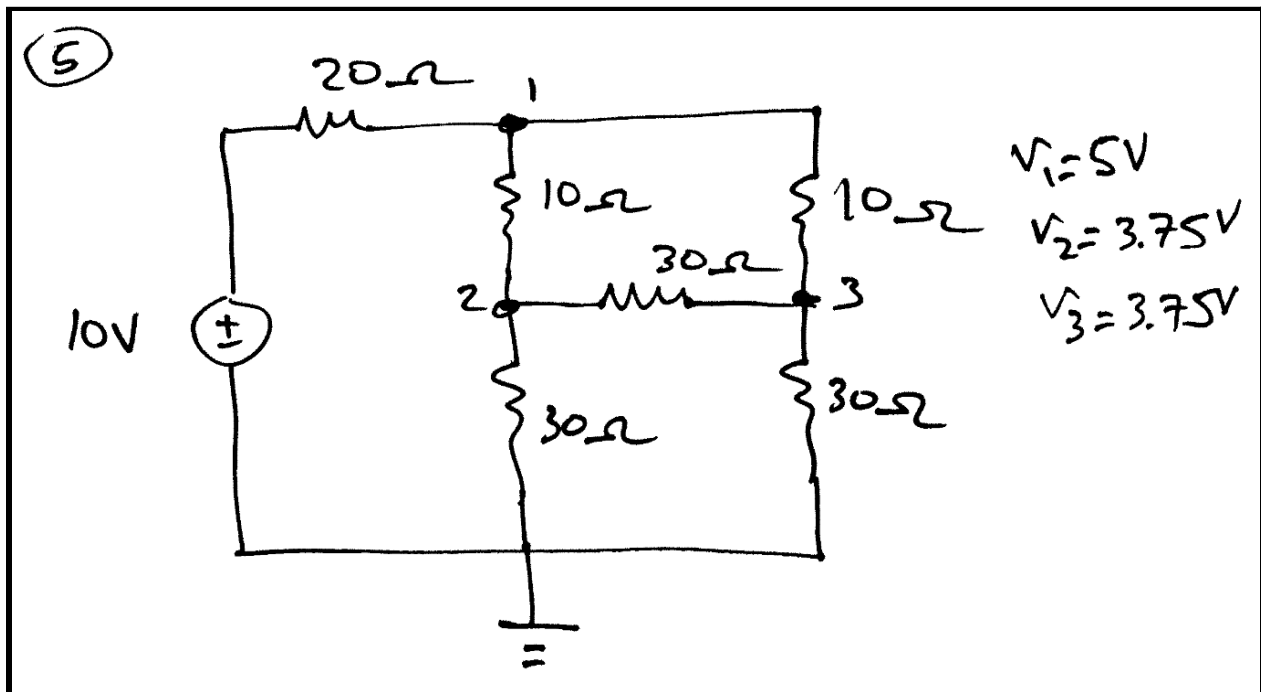


Result:

```
julia> solve_circuit(circuit5...)
3×1 Matrix{Float64}:
 5.000000000000001
 3.7500000000000004
 3.750000000000001
```

Question 2: Take a regular N-by-2N finite-difference mesh and replace each horizontal and vertical line by a 1-kΩ resistor. This forms a linear, resistive network.

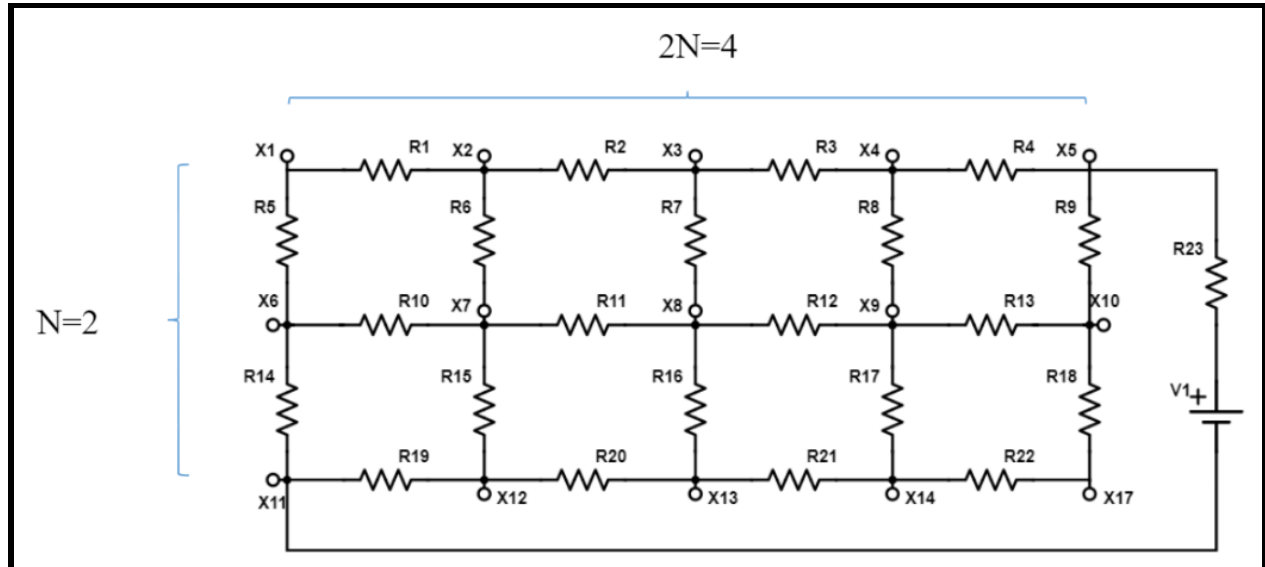- a) Using the program you developed in question 1, find the resistance, R , between the node at the bottom-left corner of the mesh and the node at the top right corner of the mesh, for $N = 2, 3, \dots, 10$. (You will probably want to write a small program that generates the input file needed by the network analysis program. Constructing by hand the incidence matrix for a 200-node network is rather tedious).

A function was created to generate the key matrices and vectors for defining a circuit configuration for an N-by-2N finite-difference mesh, like shown in the diagram below.



To determine the equivalent resistance, a branch is added by the function, connecting the top-right corner to the bottom-left, with a voltage source and a resistor. By calculating the voltage across the network, the current through the driving branch is calculated. With the current and the voltage, the equivalent resistance was calculated using Ohm's Law. The results for N from 2 to 10 are shown in the table below.


N	Equivalent Resistance (Ω)
2	2057.416268
3	2497.718031
4	2827.490806
5	3090.573861
6	3309.185198
7	3496.083544
8	3659.251365
9	3804.006422
10	3934.065475

- b) In theory, how does the computer time taken to solve this problem increase with N , for large N ? Are the timings you observe for your practical implementation consistent with this? Explain your observations.


Choleski decomposition is $O(n^3)$, where n refers to the size of the matrix. However, because the time complexity we want for this is in terms of N , where N is the size of the finite-difference mesh, we need the complexity of n , the matrix size, with regards to N , the circuit size. Because the size of matrix A in $Ax=b$ is $n \times n$, where n is the number of nodes (each element of x

represents the voltage at one node), and there are $n = (N + 1)(2N + 1) = 2N^2 + 3N + 1$ nodes, the time complexity of solving the circuit is $O(n^3) = O((2N^2 + 3N + 1)^3) = O(N^6)$.

For the practical implementation, the results for N from 1 to 32 are plotted below, as well as plotted vs N^6 , with the raw results shown further below. The observed timings appear to be generally consistent with the theoretical, with the only caveat that individual timings for samples vary, depending on the just-in-time compile time of the Julia programming language. This can be seen in the raw results, where it reports the percentage that is “gc time”.

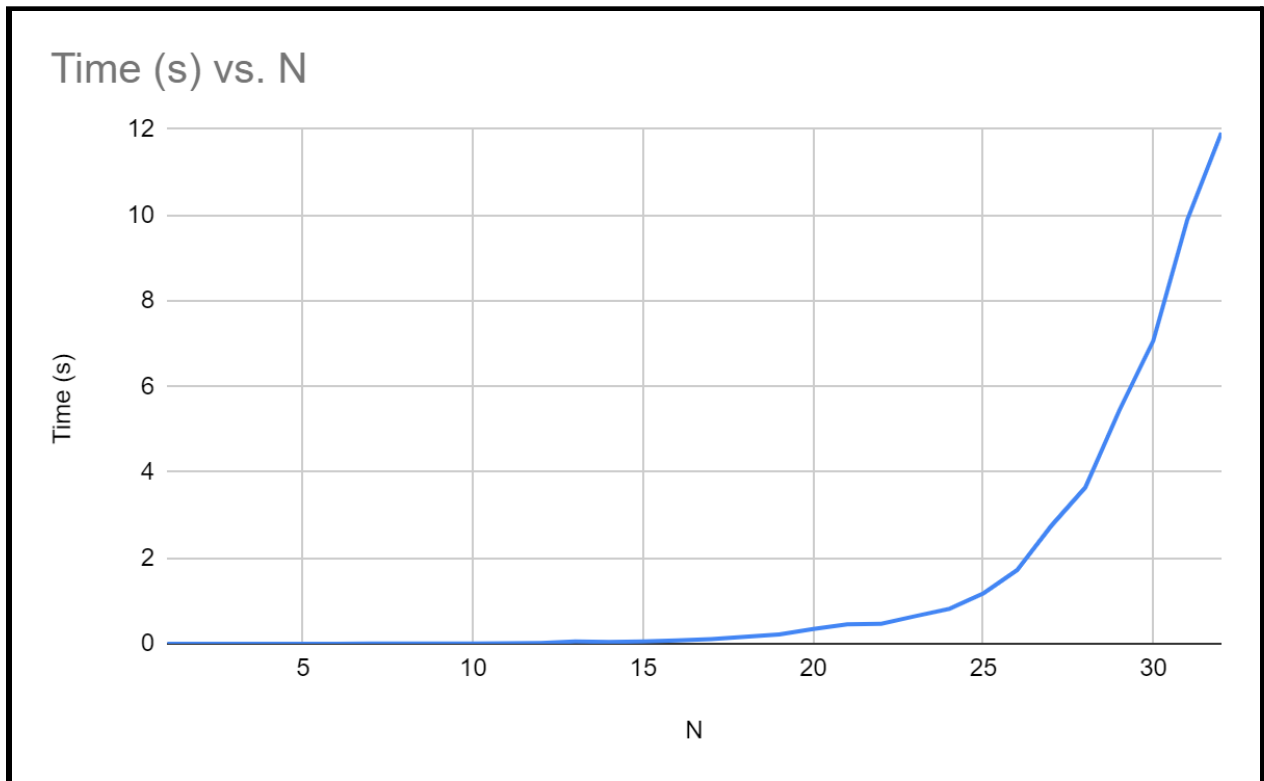

Time(s) vs N^6

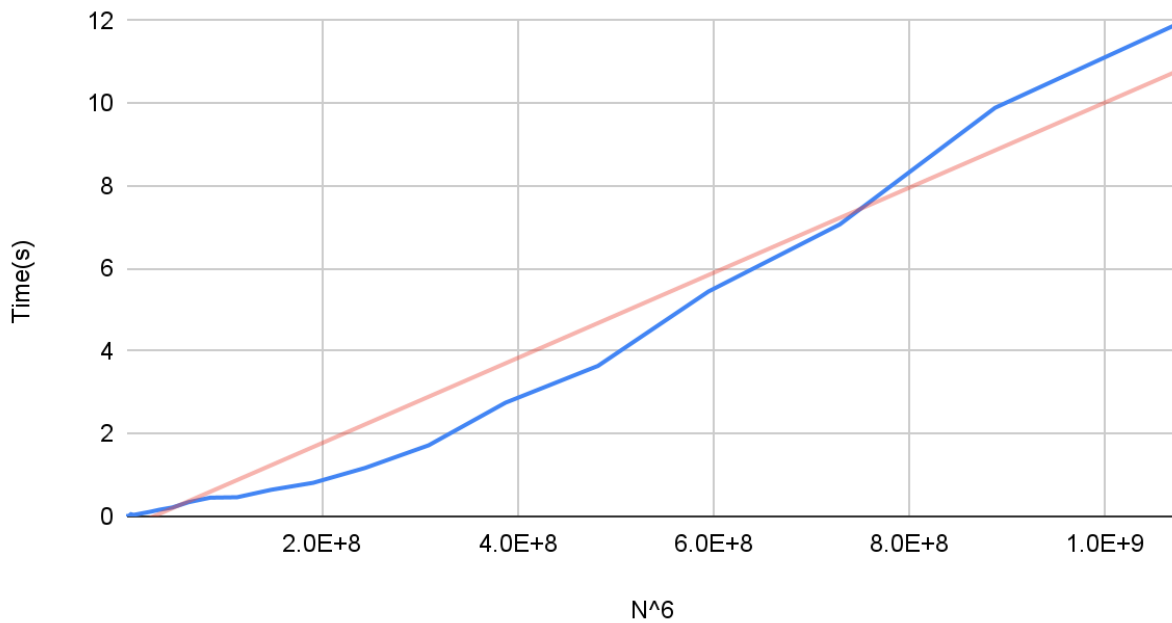

```

N = 1      0.000013 seconds (9 allocations: 2.219 KiB)
N = 2      0.000016 seconds (9 allocations: 11.625 KiB)
N = 3      0.000041 seconds (10 allocations: 40.031 KiB)
N = 4      0.000083 seconds (11 allocations: 106.281 KiB)
N = 5      0.000245 seconds (13 allocations: 234.297 KiB)
N = 6      0.000567 seconds (13 allocations: 454.484 KiB)
N = 7      0.001105 seconds (13 allocations: 802.844 KiB)
N = 8      0.002290 seconds (13 allocations: 1.290 MiB)
N = 9      0.006104 seconds (13 allocations: 2.009 MiB)
N = 10     0.005483 seconds (13 allocations: 2.994 MiB)
N = 11     0.010728 seconds (13 allocations: 4.303 MiB)
N = 12     0.015066 seconds (13 allocations: 6.002 MiB)
N = 13     0.052642 seconds (13 allocations: 8.160 MiB, 50.43% gc time)
N = 14     0.037217 seconds (13 allocations: 10.854 MiB)
N = 15     0.052096 seconds (13 allocations: 14.166 MiB)
N = 16     0.077089 seconds (13 allocations: 18.184 MiB)
N = 17     0.109164 seconds (13 allocations: 23.001 MiB)
N = 18     0.160886 seconds (13 allocations: 28.718 MiB, 6.47% gc time)
N = 19     0.215193 seconds (13 allocations: 35.440 MiB, 8.31% gc time)
N = 20     0.344996 seconds (13 allocations: 43.279 MiB, 22.39% gc time)
N = 21     0.452820 seconds (13 allocations: 52.351 MiB, 13.35% gc time)
N = 22     0.463546 seconds (13 allocations: 62.780 MiB, 0.60% gc time)

```


```

N = 23    0.643390 seconds (15 allocations: 74.695 MiB, 0.51% gc time)
N = 24    0.812997 seconds (15 allocations: 88.230 MiB, 0.40% gc time)
N = 25    1.173516 seconds (15 allocations: 103.527 MiB, 0.85% gc time)
N = 26    1.720299 seconds (15 allocations: 120.732 MiB, 0.56% gc time)
N = 27    2.751907 seconds (15 allocations: 139.997 MiB, 3.09% gc time)
N = 28    3.642942 seconds (15 allocations: 161.481 MiB, 0.31% gc time)
N = 29    5.444953 seconds (15 allocations: 185.348 MiB, 0.06% gc time)
N = 30    7.069585 seconds (15 allocations: 211.768 MiB, 0.28% gc time)
N = 31    9.890783 seconds (15 allocations: 240.917 MiB, 0.26% gc time)
N = 32   11.919678 seconds (18 allocations: 272.975 MiB, 0.25% gc time)


```

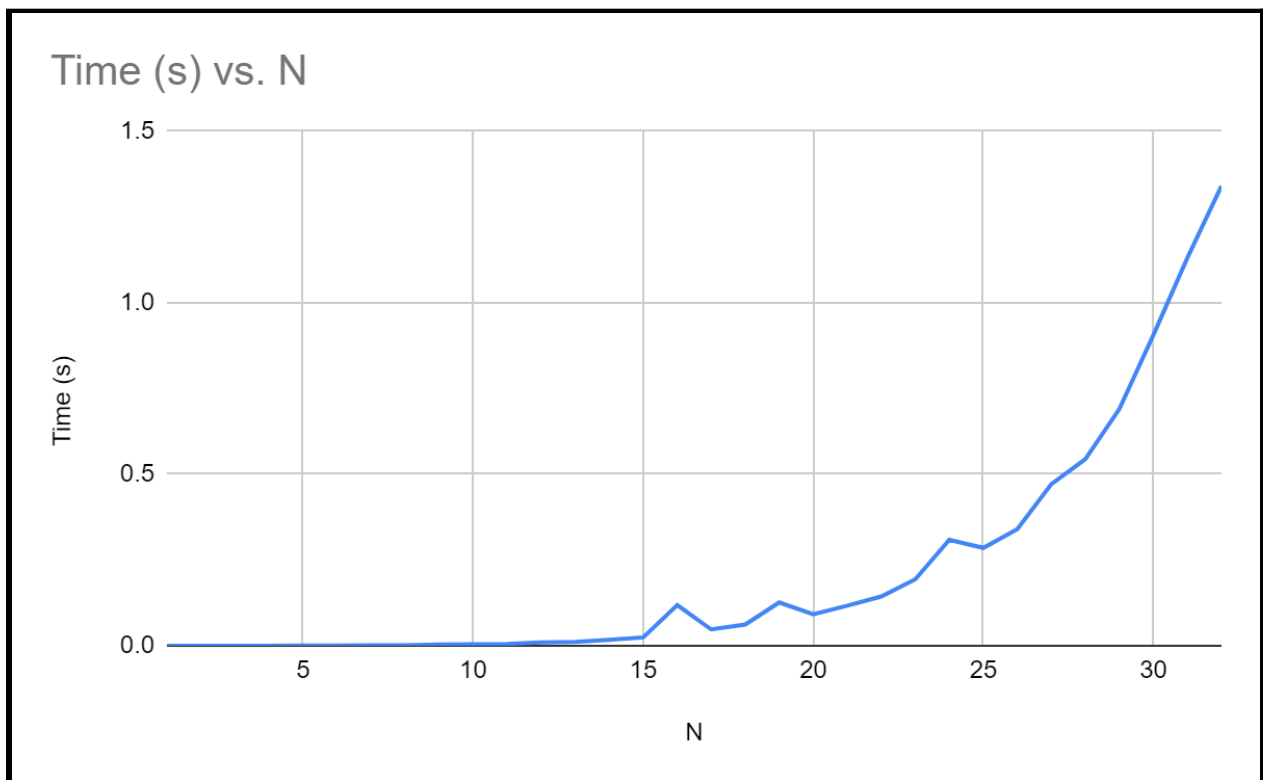c) Modify your program to exploit the sparse nature of the matrices to save computation time. What is the half-bandwidth b of your matrices? In theory, how does the computer time taken to solve this problem increase now with N , for large N ? Are the timings for your practical sparse implementation consistent with this? Explain your observations.

By inspecting the matrices, the halfband $b = 2N + 2$. The complexity, then, of Cholesky decomposition is $O(b^2n) = O((4N^2 + 8N + 4)(2N^2 + 3N + 1)) = O(N^4)$. As can be seen in the plots below, the experimental results are generally consistent with the theory, with the same caveat as for without halfbanding.



Time (s) vs. N^4

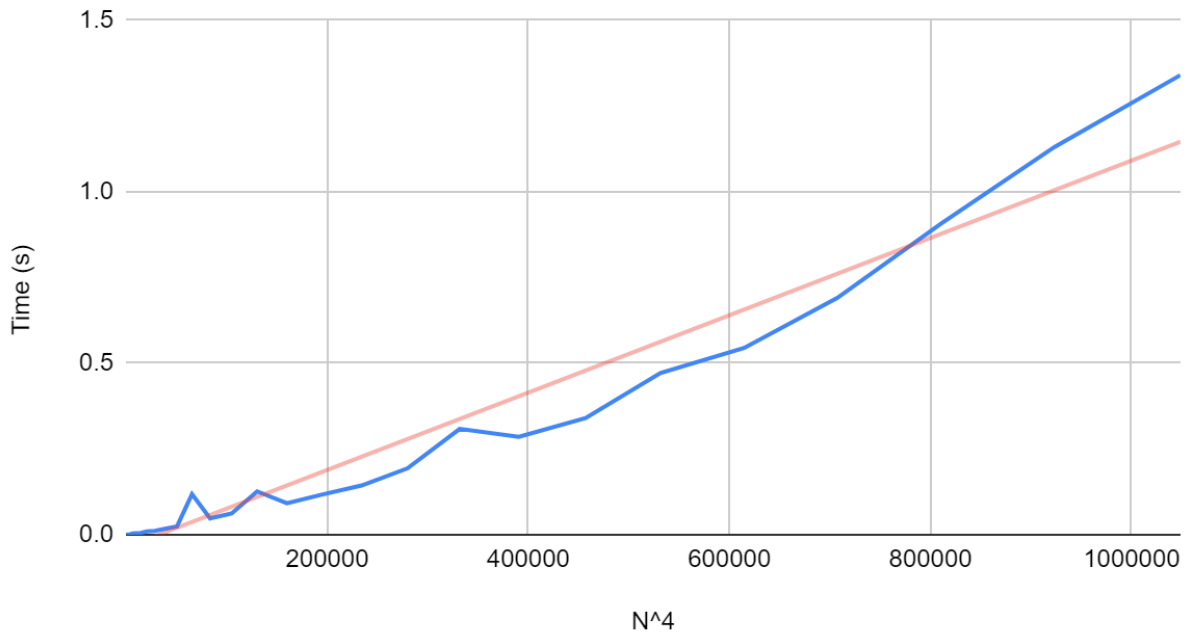

```

N = 1  b = 4      0.000012 seconds (10 allocations: 2.234 KiB)
N = 2  b = 6      0.000015 seconds (10 allocations: 11.641 KiB)
N = 3  b = 8      0.000032 seconds (11 allocations: 40.047 KiB)
N = 4  b = 10     0.000074 seconds (12 allocations: 106.297 KiB)
N = 5  b = 12     0.000260 seconds (14 allocations: 234.312 KiB)
N = 6  b = 14     0.000436 seconds (14 allocations: 454.500 KiB)
N = 7  b = 16     0.000852 seconds (14 allocations: 802.859 KiB)
N = 8  b = 18     0.001327 seconds (14 allocations: 1.290 MiB)
N = 9  b = 20     0.003338 seconds (14 allocations: 2.009 MiB)
N = 10 b = 22     0.004488 seconds (14 allocations: 2.994 MiB)
N = 11 b = 24     0.005189 seconds (14 allocations: 4.303 MiB)
N = 12 b = 26     0.009716 seconds (14 allocations: 6.002 MiB)
N = 13 b = 28     0.011336 seconds (14 allocations: 8.160 MiB)
N = 14 b = 30     0.017198 seconds (14 allocations: 10.854 MiB)
N = 15 b = 32     0.024166 seconds (14 allocations: 14.166 MiB)
N = 16 b = 34     0.118487 seconds (14 allocations: 18.184 MiB, 71.00% gc
time)
N = 17 b = 36     0.047366 seconds (14 allocations: 23.001 MiB)
N = 18 b = 38     0.061710 seconds (14 allocations: 28.718 MiB)
N = 19 b = 40     0.126183 seconds (14 allocations: 35.440 MiB, 45.87% gc
time)
N = 20 b = 42     0.091651 seconds (14 allocations: 43.279 MiB, 5.11% gc

```

```


time)
N = 21  b = 44      0.116694 seconds (14 allocations: 52.351 MiB, 4.56% gc
time)
N = 22  b = 46      0.143454 seconds (14 allocations: 62.780 MiB, 4.40% gc
time)
N = 23  b = 48      0.193593 seconds (16 allocations: 74.695 MiB, 3.39% gc
time)
N = 24  b = 50      0.308600 seconds (16 allocations: 88.230 MiB, 1.59% gc
time)
N = 25  b = 52      0.285202 seconds (16 allocations: 103.527 MiB, 1.28% gc
time)
N = 26  b = 54      0.339835 seconds (16 allocations: 120.732 MiB, 1.29% gc
time)
N = 27  b = 56      0.471387 seconds (16 allocations: 139.997 MiB, 2.85% gc
time)
N = 28  b = 58      0.544305 seconds (16 allocations: 161.481 MiB, 1.01% gc
time)
N = 29  b = 60      0.690168 seconds (16 allocations: 185.348 MiB, 0.91% gc
time)
N = 30  b = 62      0.905897 seconds (16 allocations: 211.768 MiB, 7.27% gc
time)
N = 31  b = 64      1.130770 seconds (16 allocations: 240.917 MiB, 1.93% gc
time)
N = 32  b = 66      1.340049 seconds (19 allocations: 272.975 MiB, 0.43% gc
time)

```

d) Plot a graph of R versus N. Find a function $R(N)$ that fits the curve reasonably well and is asymptotically correct as N tends to infinity, as far as you can tell.

Below is a plot of equivalent resistance, R, vs N. Included is a logarithmic trendline, with function $R(N) = 1219 + 1172\ln(N)$. As shown below, the trendline has an R^2 value of 0.999, suggesting a very strong fit, as is also visible by how closely the trendline tracks the observed results.

Equivalent Resistance (Ω) vs. N

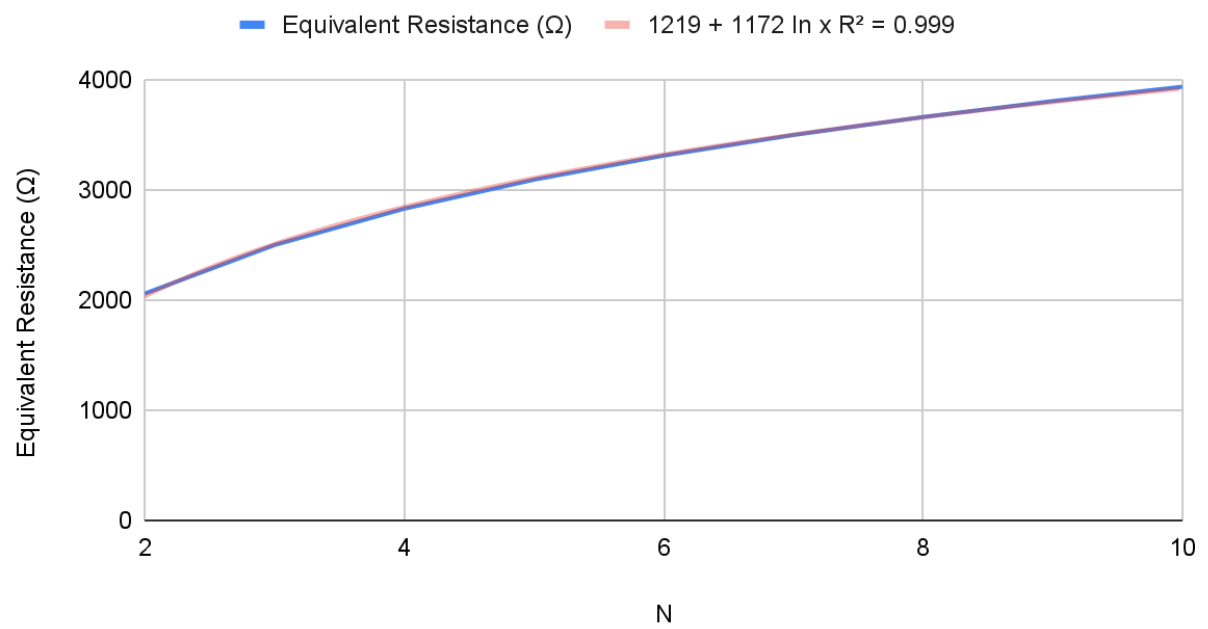

Question 3: Figure 1 shows the cross-section of an electrostatic problem with translational symmetry: a coaxial cable with a square outer conductor and a rectangular inner conductor. The inner conductor is held at 15 volts and the outer conductor is grounded.

- Write a computer program to find the potential at the nodes of a regular mesh in the air between the conductors by the method of finite differences. Use a five-point difference formula. Exploit at least one of the planes of mirror symmetry that this problem has. Use an equal node-spacing, h , in the x and y directions. Solve the matrix equation by successive over-relaxation (SOR), with SOR parameter ω . Terminate the iteration when the magnitude of the residual at each free node is less than 10^{-5} .
- With $h = 0.02$, explore the effect of varying ω . For 10 values of ω between 1.0 and 2.0, tabulate the number of iterations taken to achieve convergence, and the corresponding value of potential at the point $(x, y) = (0.06, 0.04)$. Plot a graph of number of iterations versus ω .

Appendix

choleski.jl

```
using Test

"""
Uses Choleski decomposition to solve `Ax = b`, where A is real, symmetric,
and positive-definite. Returns the vector x.
"""
function choleski(A::AbstractMatrix{<:Real}, b::AbstractVector{<:Real},
halfband=nothing)
    n, m = size(A)

    # simple error checking
    if n != m
        throw(DimensionMismatch("Matrix A must be square"))
    elseif length(b) != n
```

```

        throw(DimensionMismatch("Matrix A must be n×n, and vector b must be
n×1"))
    end

    # initialize
    L = zeros(n,n)
    y = zeros(n,1)
    x = zeros(n,1)

    #decompose L
    for j ∈ 1:n
        sum = 0
        for q = 1:j-1
            @inbounds sum = sum + L[j,q]^2
        end
        @inbounds L[j,j] = sqrt(A[j,j] - sum )

        sumi = 0

        i_range = (j+1):n
        if !isnothing(halfband)
            if (j + halfband + 1) < n
                i_range = (j+1):(j+halfband)
            end
        end
        for i ∈ i_range

            for k ∈ 1:j-1
                if k == 1
                    @inbounds sumi = L[i,k]*L[j,k]
                else
                    @inbounds sumi = sumi + L[i,k]*L[j,k]
                end
            end
            @inbounds L[i,j] = (A[i,j] - sumi) / L[j,j]
        end
    end

    #get y
    for i ∈ 1:n
        sumy = 0
        for j ∈ 1:i-1
            @inbounds sumy = sumy + L[i,j]*y[j]

```

```

        end
        @inbounds y[i] = (b[i] - sum_y) / L[i,i]
    end
    #calculate x
    for i ∈ n:-1:1
        sum_x = 0
        for j ∈ (i+1):n
            @inbounds sum_x = sum_x + L[j,i]*x[j]
        end
        @inbounds x[i] = (y[i] - sum_x) / L[i,i]
    end

    return x
end

@testset "real, symmetric, and positive-definite" begin
    # test a simple 2x2 case
    test_A = [1 0; 0 1]
    test_x = [1; 1]
    test_b = test_A * test_x
    @test choleski(test_A, test_b) ≈ test_x # approx is to account for
floating point errors

    # test 10 random 2x2 cases
    for i ∈ 1:10
        test_x = rand(2)
        test_b = test_A * test_x
        @test choleski(test_A, test_b) ≈ test_x
    end

    # test a simple 3x3 case
    test_A = [2 -1 0; -1 2 -1; 0 -1 2]
    test_x = [1; 1; 1]
    test_b = [1; 0; 1]
    @test choleski(test_A, test_b) ≈ test_x

    # test 10 random 3x3 cases
    for i ∈ 1:10
        test_x = rand(3)
        test_b = test_A * test_x
        @test choleski(test_A, test_b) ≈ test_x
    end
end
end

```


circuit.jl

```
using TOML

"""
Retrieves a circuit of a given ID and returns its reduced incidence matrix,
A; current source matrix, J;
resistance matrix, R; and voltage source matrix, E. These are returned as a
named tuple.
"""
function get_circuit(id::Int)
    circuit = TOML.parsefile("Assignment 1/circuits/circuit$(id).toml")

    # return as named tuple
    # need to flatten A into a matrix instead of nested vectors
    return (A = transpose(hcat(circuit["A"]...)), J = circuit["J"], R =
circuit["R"], E = circuit["E"])
end

"""
Solves a circuit given the reduced incidence matrix, A; current source
matrix, J;
resistance matrix, R; and voltage source matrix, E. Solves using Choleski
decomposition.

Tip: use the spread operator, `...`, to use the returned output of
`get_circuit(id)`
without having to access the members of the named tuple.
"""
function solve_circuit(A, J, R, E, halfband=nothing)
    #  $(A Y A^T) v = A (J - Y E)$ 

    # fill in Y with zeros everywhere but the main diagonal
    Y = zeros(length(R), length(R))
    for i ∈ 1:length(R)
        Y[i,i] = 1.0 / R[i]
    end

    # perform choleski decomposition with constructed A and b
    v = choleski(A * Y * transpose(A), A * (J - (Y * E)), halfband)
    return v
end

"""
```

Generates an $N \times 2N$ finite-difference mesh where each branch is a resistor of given resistance.

It also has attached a branch connecting the top-right node to the bottom-left node

with a voltage source and resistor. This is to allow measurement of equivalent resistance.

Return value is in the same form as for ``get_circuit``, allowing easy piping into ``solve_circuit``

with the spread operator, ``...``.

"""

```
function generate_circuit(N, R, sJ, sR, sE)
```

```
    # calculate number of branches
```

```
    n_branch = (N + 1)*2*N + N*(2*N + 1)
```

```
    # construct J, R, E for the main  $N \times 2N$  mesh
```

```
    J = zeros(n_branch)
```

```
    R = R * ones(n_branch)
```

```
    E = zeros(n_branch)
```

```
    # add voltage-source branch for testing equivalent resistance across  
the mesh
```

```
    push!(J, sJ)
```

```
    push!(R, sR)
```

```
    push!(E, sE)
```

```
    # calculate nodes
```

```
    n_node = (N + 1) * (2*N + 1)
```

```
    # zero-initialize A
```

```
    A = zeros(n_node, n_branch + 1)
```

```
    #print len(A), len(A[0])
```

```
    # set all the correct values in A
```

```
    for i_node ∈ 1:n_node
```

```
        # level = which row within the mesh, 1-indexed
```

```
        level = ((i_node - 1) ÷ (2*N + 1)) + 1
```

```
        # offset = which column within the mesh, 1-indexed
```

```
        offset = ((i_node - 1) % (2*N + 1)) + 1
```

```
        branch_per_level = 2*N + (2*N + 1)
```

```

# calculate surrounding branch indices
right = branch_per_level * (level - 1) + offset
left = right - 1
top = right - (2*N + 1)
bottom = top + branch_per_level
#print i, 'r',right, 'l', left, 't',top, 'b', bottom

# node on top border
if level == 1
    # top left
    if offset == 1
        A[i_node, right], A[i_node, bottom] = -1, 1
    # top right
    elseif offset == (2*N + 1)
        A[i_node, left], A[i_node, bottom] = 1, 1
    else
        A[i_node, right], A[i_node, left], A[i_node, bottom] = -1,
1, 1
    end
# node on bottom border
elseif level == (N + 1)
    # bottom left
    if offset == 1
        A[i_node, right], A[i_node, top] = -1, -1
    # bottom right
    elseif offset == (2*N + 1)
        A[i_node, top], A[i_node, left] = -1, 1
    else
        A[i_node, right], A[i_node, top], A[i_node, left] = -1,
-1, 1
    end
# node on left border
elseif offset == 1
    A[i_node, right], A[i_node, top], A[i_node, bottom] = -1, -1,
1
# node on right border
elseif offset == (2*N + 1)
    A[i_node, top], A[i_node, left], A[i_node, bottom] = -1, 1, 1
# nodes in middle
else
    A[i_node, right], A[i_node, top], A[i_node, left], A[i_node,
bottom] = -1, -1, 1, 1

```

```

        end

        # setup the voltage source
        # right top corner
        if level == 1 && offset == (2*N + 1)
            A[i_node, n_branch + 1] = -1
        elseif level == (N + 1) && offset == 1
            A[i_node, n_branch + 1] = 1
        end
    end
end

# set up ground node by removing that node from A
# i.e., remove the row from A corresponding to the bottom-left corner
node
A = A[setdiff(1:end, N*(2*N + 1) + 1), :]

return (A = A, J = J, R = R, E = E)
end

```

main.jl

```

include("Assignment 1/choleski.jl")
include("Assignment 1/circuit.jl")

# solve circuit 1 from /circuits/circuit1.toml
circuit1 = get_circuit(1)
solve_circuit(circuit1...)

# solve circuit 2 from /circuits/circuit2.toml
circuit2 = get_circuit(2)
solve_circuit(circuit2...)

# solve circuit 3 from /circuits/circuit3.toml
circuit3 = get_circuit(3)
solve_circuit(circuit3...)

# solve circuit 4 from /circuits/circuit4.toml
circuit4 = get_circuit(4)
solve_circuit(circuit4...)

# solve circuit 5 from /circuits/circuit5.toml
circuit5 = get_circuit(5)
solve_circuit(circuit5...)

```

```

# solve N×2N finite-difference mesh for N = 2
R, sJ, sR, sE = 1000, 0, 1000, 100
R_equivalent = []
for N ∈ 1:32
    circuit_mesh = generate_circuit(N, R, sJ, sR, sE)
    halfband = 2*N + 2
    print("N = $N\tb = $halfband\t")
    @time v_mesh = solve_circuit(circuit_mesh..., halfband)
    v₁ = v_mesh[2*N + 1]
    v₂ = 0
    I = ((v₂ + sE) - v₁) / sR
    R_mesh = (v₁ - v₂) / I

    push!(R_equivalent, R_mesh)
end

```

References

https://en.wikipedia.org/wiki/Definite_matrix#Examples
<https://toml.io/en/>
<https://github.com/JuliaLang/TOML.jl>